

Principles Of Digital Design

Chapter 3

Boolean Algebra and Logic Design

- *Boolean Algebra*
- *Logic Gates*
- *Digital Design*
- *Implementation Technology*
 - ◆ *ASICs*
 - ◆ *Gate Arrays*

Basic Algebraic Properties

- A set is a collection of objects with a common property
 - ♦ If S is a set and x is a member of the set S , then $x \in S$
 - $A = \{1, 2, 3, 4\}$ denotes the set A , whose elements are 1, 2, 3, 4
- A binary operator on a set S is a rule that assigns to each pair of elements in S another element that is in S
- Axioms are assumption that are valid without proof

Examples of Axioms

• Closure

- ♦ A set S is closed with respect to a binary operator \bullet iff for all $x, y \in S$,
 $(x \bullet y) \in S$
 - $Z^+ = \{1, 2, 3, \dots\}$ is closed to addition, because positive numbers are in Z^+

• Associativity

- ♦ A binary operator \bullet defined on a set S is associative iff for all
 $x, y, z \in S$

$$(x \bullet y) \bullet z = x \bullet (y \bullet z)$$

• Identity Element

- ♦ A set S has an identity element e for every $x \in S$

$$e \bullet x = x \bullet e = x$$

$$x + 0 = 0 + x = x$$

Examples of Axioms

• Commutativity

- ♦ A binary operator \bullet is commutative iff for all $x, y \in S$

$$x \bullet y = y \bullet x$$

• Inverse Element

- ♦ A set S has an inverse iff for every $x \in S$, there exists an element $y \in S$ such that

$$x \bullet y = e$$

• Distributivity

- ♦ If \bullet and \square are two binary operators on a set S , \bullet is said to be distributive over \square if, for all $x, y, z \in S$

$$x \bullet (y \square z) = (x \bullet y) \square (x \bullet z)$$

Axiomatic Definition of Boolean Algebra

Boolean algebra is a set of elements B with two binary operators, $+$ and \cdot , which satisfies the following six axioms:

- **Axiom 1 (Closure Property):** (a) B is closed with respect to the operator $+$; (b) B is also closed with respect to the operator \cdot
- **Axiom 2 (Identity Element):** (a) B has an identity element with respect to $+$, designated by 0 ; (b) B also has an identity element with respect to \cdot , designated by 1
- **Axiom 3 (Commutativity Property):** (a) B is commutative with respect to $+$; (b) B is also commutative with respect to \cdot
- **Axiom 4 (Distributivity Property):** (a) The operator \cdot is distributive over $+$; (b) similarly, the operator $+$ is distributive over \cdot
- **Axiom 5 (Complement Element):** For every $x \in B$, there exists an element $x' \in B$ such that (a) $x + x' = 1$ and (b) $x \cdot x' = 0$
This second element x' , is called the complement of x
- **Axiom 6 (Lower Cardinality Bound):** There are at least two elements $x, y \in B$ such that $x \neq y$

Axiomatic Definition of Boolean Algebra

Differences between Boolean algebra and ordinary algebra

- In ordinary algebra, $+$ is not distributive \cdot
- Boolean algebra does not have inverses with respect to $+$ and \cdot ; therefore, there are no subtraction or division operations in Boolean algebra
- Complements are available in Boolean algebra, but not in ordinary algebra
- Boolean algebra applies to a finite set of elements, whereas ordinary algebra would apply to the infinite sets of real numbers
- The definition above for Boolean algebra does not include associativity, since it can be derived from the other axioms

Two-valued Boolean Algebra

- Set B has two elements: 0 and 1
- Algebra has two operators: AND and OR

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

AND Operator

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR Operator

Two-valued Boolean Algebra

Two-valued Boolean algebra satisfies Huntington axioms

- **Axiom 1 (Closure Property):** Closure is evident in the AND/OR tables, since the result of each operation is an element of B .
- **Axiom 2 (Identity Element):** The identity elements in this algebra are 0 for the operator $+$ and 1 for the operator \cdot . From the AND/OR tables, we see that:
 - ◆ $0 + 0 = 0$, and $0 + 1 = 1 + 0 = 1$
 - ◆ $1 \cdot 1 = 1$, and $1 \cdot 0 = 0 \cdot 1 = 0$
- **Axiom 3 (Commutativity Property):** The commutativity laws follow from the symmetry of the operator tables.

Two-valued Boolean Algebra

- **Axiom 4 (Distributivity):** The distributivity of this algebra can be demonstrated by checking both sides of the equation.

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$x + (y \cdot z) = (x + y)(x + z).$$

x	y	z	y + z	x · (y + z)	xy	xz	(xy) + (xz)
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

x	y	z	yz	x + (yz)	x + y	x + z	(x + y)(x + z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

Proof of distributivity of ·

Proof of distributivity of +

Two-valued Boolean Algebra

- **Axiom 5 (Complement):** 0 and 1 are complements of each other, since $0 + 0' = 0 + 1 = 1$ and $1 + 1' = 1 + 0 = 1$; furthermore, $0 \cdot 0' = 0 \cdot 1 = 0$ and $1 \cdot 1' = 1 \cdot 0 = 0$.

x	x'
0	1
1	0

NOT Operator

- **Axiom 6 (Cardinality):** The cardinality axiom is satisfied, since this two-valued Boolean algebra has two distinct elements, 1 and 0, and $1 \neq 0$.

Boolean Operator Procedure

- Boolean operators are applied in the following order.

- ◆ Parentheses ()
- ◆ NOT ' (prime)
- ◆ AND . (dot)
- ◆ OR + (plus)

Example: Evaluate expression $(x + xy)'$ for $x = 1$ and $y = 0$:

$$(1 + 1 \cdot 0)' = (1 + 0)' = (1)' = 0$$

Duality Principle

- Any algebraic expression derived from axioms stays valid when

- ♦ OR and AND
- ♦ 0 and 1

are interchanged.

Example:

If

$$X + 1 = 1$$

then

$$X \cdot 0 = 0$$

by the duality principle

Theorem of Boolean Algebra

Theorem 1	(a)	$x + x = x$
(Idempotency)	(b)	$xx = x$
Theorem 2	(a)	$x + 1 = 1$
	(b)	$x \cdot 0 = 0$
Theorem 3	(a)	$yx + x = x$
(Absorption)	(b)	$(y + x)x = x$
Theorem 4		$(x')' = x$
(Involution)		
Theorem 5	(a)	$(x + y) + z = x + (y + z)$
(Associativity)	(b)	$x(yz) = (xy)z$
Theorem 6	(a)	$(x + y)' = x'y'$
(De Morgan's Law)	(b)	$(xy)' = x' + y'$

Basic Theorems of Boolean Algebra

Theorem Proofs in Boolean Algebra

- Theorems can be proved by transformations based on axioms and theorems

Example:

Theorem 1(a) Idempotency: $x + x = x$.

Proof:

$$\begin{aligned}x + x &= (x + x) \cdot 1 && \text{by identity (Ax. 2b)} \\ &= (x + x) (x + x') && \text{by complement (Ax. 5a)} \\ &= x + xx' && \text{by distributivity (Ax. 4b)} \\ &= x + 0 && \text{by complement (Ax. 5b)} \\ &= x && \text{by identity (Ax. 2a)}\end{aligned}$$

- Duality

Example:

Theorem 1(b) Idempotency: $x \cdot x = x$.

Proof:

$$\begin{aligned}x + x &= x && \text{by Theorem 1(a)} \\ x \cdot x &= x && \text{by Duality principle}\end{aligned}$$

Theorem Proofs in Boolean Algebra

- Checking theorems for every combinations of variable value

Example:

Theorem 6(a) DeMorgan's Law: $(x + y)' = x'y'$

x	y	$x + y$	$(x + y)'$	x'	y'	$x'y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

Proof of Demorgan's First Theorem

Boolean Functions

- Algebraic expression, which are formed from binary variables and Boolean operators AND, OR and NOT.

Example:

$$F_1 = xy + xy'z + x'yz$$

This function would be equal to 1 if $x = 1$ and $y = 1$, or
if $x = 1$ and $y = 0$ and $z = 1$, or
if $x = 0$ and $y = 1$ and $z = 1$;

otherwise, $F_1 = 0$.

Note 1: When we evaluate Boolean expressions, we must follow a specific order of operations, namely, (1) parentheses, (2) NOT, (3) AND, (4) OR.

Note 2: A primed or unprimed variable is usually called a literal.

Boolean Functions

- Truth tables which list the functional value for all combinations of variable values.

Example:

$$F_1 = xy + xy'z + x'yz$$

Row Numbers	Variable Values			Function Values
	x	y	z	F_1
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Complement of a Function

- Complement of function F is function F' , where F' can be obtained by:

♦ Interchanging 0 and 1 in the truth table.

Example:

$$F_1 = xy + xy'z + x'yz$$

Row Numbers	Variable Values			Function Values	
	x	y	z	F_1	F_1'
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	0

Complement of a Function

- Complement of function F is function F' , where F' can be obtained by:

- ♦ Repeatedly applying DeMorgan's theorems.

Example:


$$\begin{aligned}
 F_1' &= (xy + xy'z + x'yz)' && \text{by definition of } F' \\
 &= (xy)'(xy'z)'(x'yz)' && \text{by DeMorgan's Th.} \\
 &= (x' + y')(x' + y + z')(x + y' + z') && \text{by DeMorgan's Th.}
 \end{aligned}$$

- ♦ Duality Principle

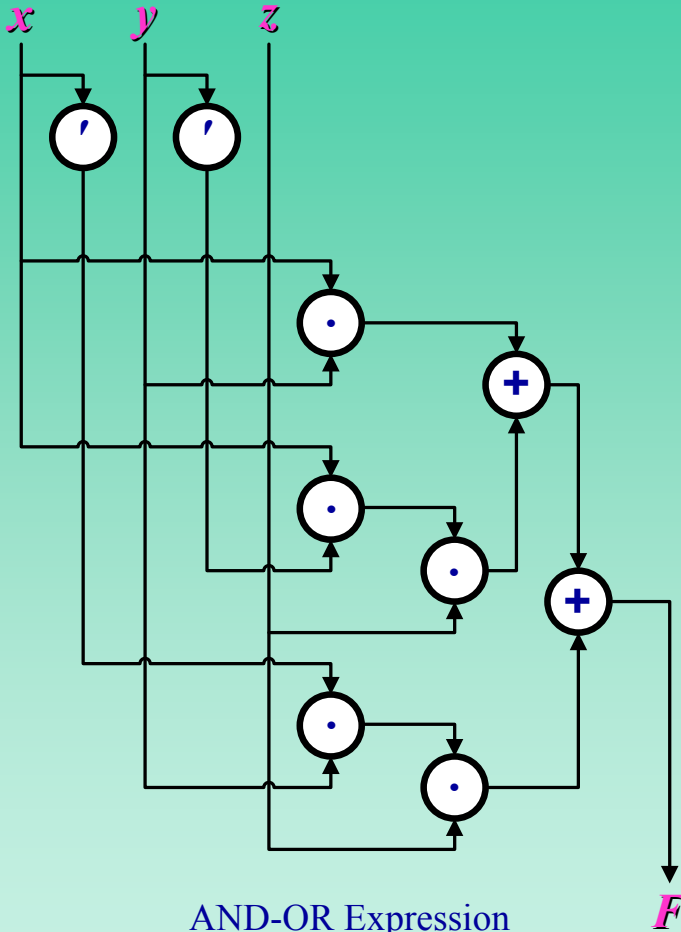Example:


$$\begin{aligned}
 F_1 &= (x \cdot y) + (x \cdot y' \cdot z) + (x' \cdot y \cdot z) \\
 &\quad \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \\
 F_1' &= (x' + y') \cdot (x' + y + z') \cdot (x + y' + z')
 \end{aligned}$$

Graphic Representation of Boolean Functions



AND-OR Expression

F size = 5 ANDs
2 ORs
2 NOTs

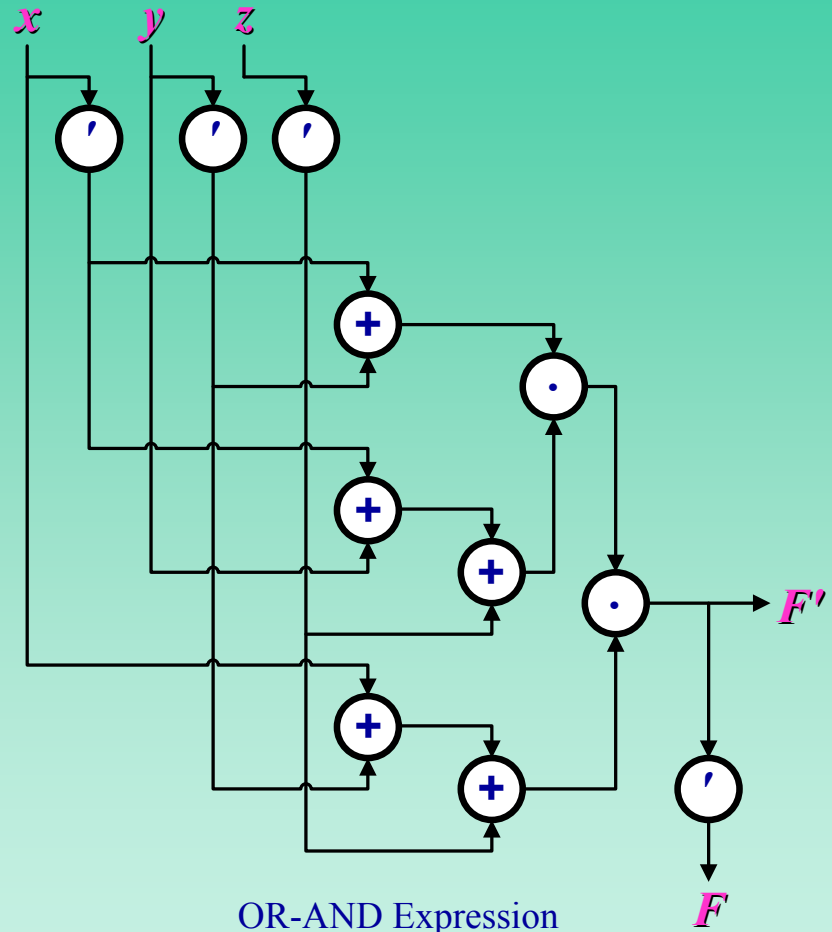

OR-AND Expression

F size = 2 ANDs
5 ORs
4 NOTs

Two different expressions have different sizes

Expression Equivalence

- We can prove expression equivalence by algebraic manipulation in which each transformation uses an axiom or a theorem of Boolean algebra.

Example:

$$F_1 = xy + xy'z + x'yz$$

$$= xy + xz + yz$$

Proof:

$xy + xy'z + x'yz$	$= xy + xyz + xy'z + x'yz$	by absorption
	$= xy + x(y + y')z + x'yz$	by distributivity
	$= xy + x1z + x'yz$	by complement
	$= xy + xz + x'yz$	by identity
	$= xy + xyz + xz + x'yz$	by absorption
	$= xy + xz + (x + x')yz$	by distributivity
	$= xy + xz + 1yz$	by complement
	$= xy + xz + yz$	by identity

$xy + xy'z + x'yz$	requires 5 ANDs	2 ORs	2 NOTs
$xy + xz + yz$	requires 3 ANDs	2 ORs	
Difference:	2 ANDs	and	2 NOTs

Minterms

- Minterm definition

If $i = b_{n-1} \dots b_0$ is a binary number between 0 and $2^n - 1$, then a minterm of n variables $x_{n-1}, x_{n-2}, \dots, x_0$, could be represented as:

$$m_i(x_{n-1}, x_{n-2}, \dots, x_0) = y_{n-1} \dots y_0$$

where for all k such that $0 \leq k \leq n - 1$,

$$y_k = \begin{cases} x_k & \text{if } b_k = 1 \\ x_k' & \text{if } b_k = 0 \end{cases}$$

x	y	z	Minterms	Designation
0	0	0	$x'y'z'$	m_0
0	0	1	$x'y'z$	m_1
0	1	0	$x'yz'$	m_2
0	1	1	$x'yz$	m_3
1	0	0	$xy'z'$	m_4
1	0	1	$xy'z$	m_5
1	1	0	xyz'	m_6
1	1	1	xyz	m_7

Minterms for Three Binary Variables

Sum-of-Minterms

- Any Boolean function can be expressed as a sum (OR) of its 1-minterms:

$$F(\text{list of variables}) = \Sigma(\text{list of 1-minterm indices})$$

Example:

Row Numbers	Variable Values			Function Values	
	<i>x</i>	<i>y</i>	<i>z</i>	F_1	F_1'
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	0

Equation Table

$$F_1 = xy + xy'z + x'yz$$

$$F_1' = (x' + y')(x' + y + z')(x + y' + z')$$

$$\begin{aligned} F_1(x, y, z) &= \Sigma(3, 5, 6, 7) \\ &= m_3 + m_5 + m_6 + m_7 \\ &= x'yz + xy'z + xyz' + xyz \end{aligned}$$

$$\begin{aligned} F_1'(x, y, z) &= \Sigma(0, 1, 2, 4) \\ &= m_0 + m_1 + m_2 + m_4 \\ &= x'y'z' + x'y'z + x'yz' + xy'z' \end{aligned}$$

Expansion to Sum-of-Minterms

- Any Boolean function can be expanded into a sum-of-minterms form by expanding each term with $(x + x')$ for each missing variable x .

Example:

$$\begin{aligned} F &= x + yz \\ &= x(y + y')(z + z') + (x + x')yz \\ &= xyz + xy'z + xyz' + xy'z' + xyz + x'yz \end{aligned}$$

After removing duplicates and rearranging the minterms in ascending order:

$$\begin{aligned} F &= x'yz + xy'z' + xy'z + xyz' + xyz \\ &= m_3 + m_4 + m_5 + m_6 + m_7 \\ &= \Sigma(3, 4, 5, 6, 7) \end{aligned}$$

Conversion to Sum-of-Minterms

- Each Boolean function can be converted into a sum-of-minterms form by generating the truth table and identifying 1-minterms.

Example: $F = x + yz$

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = m_3 + m_4 + m_5 + m_6 + m_7$$

Maxterms

- Maxterms can be defined as the complement of minterms:

$$M_i = m_i' \text{ and } M_i' = m_i$$

<i>x</i>	<i>y</i>	<i>z</i>	Maxterms	Designation
0	0	0	$x + y + z$	M_0
0	0	1	$x + y + z'$	M_1
0	1	0	$x + y' + z$	M_2
0	1	1	$x + y' + z'$	M_3
1	0	0	$x' + y + z$	M_4
1	0	1	$x' + y + z'$	M_5
1	1	0	$x' + y' + z$	M_6
1	1	1	$x' + y' + z'$	M_7

Maxterms for Three Binary Variables

Product-of-Maxterms

- Any Boolean function can be expressed as a product (AND) of its 0-maxterms:

$$F(\text{list of variables}) = \Pi(\text{list of 0-maxterm indices})$$

Example:

Row Numbers	Variable Values			Function Values	
	x	y	z	F_1	F_1'
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	0

Equation Table

$$F_1 = xy + xy'z + x'yz$$

$$F_1' = (x' + y')(x' + y + z')(x + y' + z')$$

$$\begin{aligned} F_1(x, y, z) &= \Pi(0, 1, 2, 4) \\ &= M_0 M_1 M_2 M_4 \\ &= (x + y + z)(x + y + z')(x + y' + z)(x' + y' + z) \end{aligned}$$

$$\begin{aligned} F_1'(x, y, z) &= \Pi(3, 5, 6, 7) \\ &= M_3 M_5 M_6 M_7 \\ &= (x + y' + z')(x' + y + z')(x' + y' + z)(x' + y' + z) \end{aligned}$$

Product-of-maxterms can also be obtained by complementing the sum-of-minterms

$$\begin{aligned} (F_1)' &= (x'yz + xy'z + xyz' + xyz)' \\ &= (x + y' + z')(x' + y + z')(x' + y' + z)(x' + y' + z) \\ &= M_3 M_5 M_6 M_7 \end{aligned}$$

$$\begin{aligned} F_1 &= (F_1')' \\ &= (x'y'z' + x'y'z + x'yz' + xyz)' \\ &= (x + y + z)(x + y + z')(x + y' + z)(x' + y' + z) \\ &= M_0 M_1 M_2 M_4 \end{aligned}$$

Expansion to Product-of-Maxterms

- Any Boolean function can be expanded into a product-of-maxterms form by expanding each term with xx' for each missing variable x .

Example:
Convert

$$\begin{aligned} F &= x'y' + xz \\ &= (x'y' + x)(x'y' + z) \\ &= (x' + x)(y' + x)(x' + z)(y' + z) \\ &= \underset{\substack{\uparrow \\ \text{missing} \\ x_i}}{(x + y')}\underset{\substack{\uparrow \\ \text{missing} \\ y_i}}{(x' + z)}\underset{\substack{\uparrow \\ \text{missing} \\ z_i}}{(y' + z)} \end{aligned}$$

Expand

$$\begin{aligned} x + y' &= x + y' + zz' = (x + y' + z)(x + y' + z') \\ x' + z &= x' + z + yy' = (x' + y + z)(x' + y' + z) \\ y' + z &= y' + z + xx' = (x + y' + z)(x' + y' + z) \end{aligned}$$

Combine

$$\begin{aligned} F &= (x + y' + z)(x + y' + z')(x' + y + z)(x' + y' + z) \\ &= M_2 M_3 M_4 M_6 = \prod(2, 3, 4, 6) \end{aligned}$$

Conversion to Product-of-Maxterms

- Any Boolean expression can be converted into a sum-of-maxterms by generating the truth table and listing all the 0-maxterms.
 - ♦ Example: $F = x'y' + xz$

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$F(x, y, z) = \Sigma(0, 1, 5, 7)$$

$$F(x, y, z) = \Pi(2, 3, 4, 6)$$

Canonical Forms

- **Two canonical forms:**
 - ◆ Sum-of-minterms
 - ◆ Product-of-maxterms
- **Canonical forms are unique.**
- **Conversion between canonical forms is achieved by:**
 - ◆ Exchanging Σ and Π
 - ◆ Listing all the missing indices

Standard Forms

- Two standard forms
 - ◆ Sum-of-products
 - ◆ Product-of-sums
- Standard forms are not unique.

- Sum-of-products is an OR expression with product terms that may have less literals than minterms

Example:

$$F = xy + x'yz + xy'z$$

Standard Forms

- **Product-of-sums is an AND expression with sum terms that may have less literals than maxterms**

Example:

$$F = (x' + y')(x + y' + z')(x' + y + z')$$

- **Standard forms have fewer operators (literals) than canonical forms**
- **Standard forms can be derived from canonical forms by combining terms that differ in one variable (this is, terms at distance 1)**

Example:

$$\begin{aligned} F_1 &= xyz + xyz' + xy'z + x'yz \\ &= xyz + xyz' + xyz + xy'z + xyz + x'yz \\ &= xy(z + z') + x(y + y')z + (x + x')yz \\ &= xy + xz + yz \end{aligned}$$


Non-standard Forms

- Non-standard forms have fewer operators (literals) than standard forms.
- They are obtained by factoring variables.

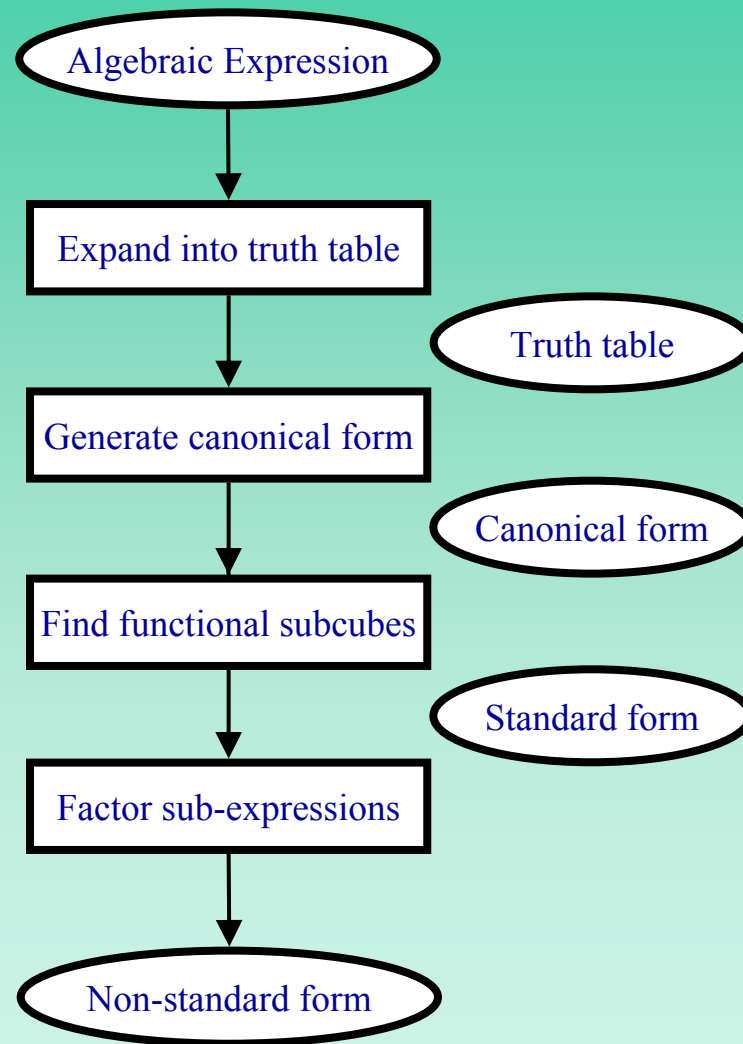Example:

$$\begin{aligned}xy + xy'z + xy'w &= x(y + y'z + y'w) \\ &= x(y + y'(z + w))\end{aligned}$$

Strategy for Operator (Literal) Reduction in Boolean Expressions











Binary Logic Operations

- There are 2^{2^n} Boolean functions for n binary variables
- Therefore, 16 Boolean functions for $n = 2$. They are

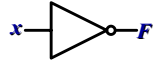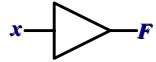Name	Operator Symbol	Functional Values for $x,y =$				Algebraic Expression	Comment
		00	01	10	11		
Zero		0	0	0	0	$F_0 = 0$	Binary constant 0
AND	$x \cdot y$	0	0	0	1	$F_1 = xy$	x and y
Inhibition	x / y	0	0	1	0	$F_2 = xy'$	x but not y
Transfer		0	0	1	1	$F_3 = x$	x
Inhibition	y / x	0	1	0	0	$F_4 = x'y$	y but not x
Transfer		0	1	0	1	$F_5 = y$	y
XOR	$x \oplus y$	0	1	1	0	$F_6 = xy' + x'y$	x or y but not both
OR	$x + y$	0	1	1	1	$F_7 = x + y$	x or y
NOR	$x \downarrow y$	1	0	0	0	$F_8 = (x + y)'$	Not-OR
Equivalence	$x \odot y$	1	0	0	1	$F_9 = xy + x'y'$	x equals y
Complement	y'	1	0	1	0	$F_{10} = y'$	Not y
Implication	$x \subset y$	1	0	1	1	$F_{11} = x + y'$	If y , then x
Complement	x'	1	1	0	0	$F_{12} = x'$	Not x
Implication	$x \supset y$	1	1	0	1	$F_{13} = x' + y$	If x , then y
NAND	$x \uparrow y$	1	1	1	0	$F_{14} = (xy)'$	Not-AND
One		1	1	1	1	$F_{15} = 1$	Binary constant 1









- There are two functions that generate constants: *Zero* and *One*. For every combination of variable values, the *Zero* function will return to 0, whereas the *One* function will return to 1.
- There are four functions of one variable, which indicate *Complement* and *Transfer* operations. Specifically, the *Complement* function will produce the complement of one of the binary variables. The *Transfer* functions by contrast will reproduce one of the binary variables at the output.
- There are ten functions that define eight specific binary operations: *AND*, *Inhibition*, *XOR*, *OR*, *NOR*, *Equivalence*, *Implication*, and *NAND*.

Digital Logic Gates

Name	Graphic Symbol	Functional Expression	Number of transistors	Delay in ns
Inverter		$F = x'$	2	1
Driver		$F = x$	4	2
AND		$F = xy$	6	2.4
OR		$F = x + y$	6	2.4
NAND		$F = (xy)'$	4	1.4
NOR		$F = (x + y)'$	4	1.4
XOR		$F = x \oplus y$	14	4.2
XNOR		$F = x \odot y$	12	3.2







Basic Logic Library
(CMOS Technology Implementations)

Multiple-Input Gates

Name	Graphic Symbol	Functional Expression	Number of transistors	Delay in <i>ns</i>
3-input AND		$F = xyz$	8	2.8
4-input AND		$F = xyzw$	10	3.2
3-input OR		$F = x + y + z$	8	2.8
4-input OR		$F = x + y + z + w$	10	3.2
3-input NAND		$F = (xyz)'$	6	1.8
4-input NAND		$F = (xyzw)'$	8	2.2
3-input NOR		$F = (x + y + z)'$	6	1.8
4-input NOR		$F = (x + y + z + w)'$	8	2.2


Multiple-Input Standard Logic Gates

Multiple-Operator (Complex) Gates

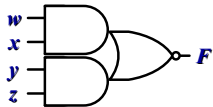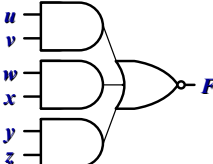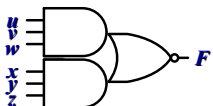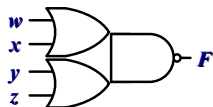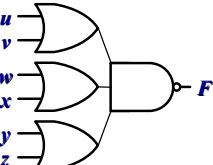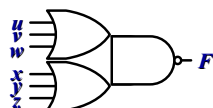Name	Graphic Symbol	Functional Expression	Number of transistors	Delay in ns
2-wide, 2-input AOI		$F = (wx + yz)'$	8	2.0
3-wide, 2-input AOI		$F = (uv + wx + yz)'$	12	2.4
2-wide, 3-input AOI		$F = (uvw + xyz)'$	12	2.2
2-wide, 2-input OAI		$F = ((w + x)(y + z))'$	8	2.0
3-wide, 2-input OAI		$F = ((u + v)(w + x)(y + z))'$	12	2.2
2-wide, 3-input OAI		$F = ((u + v + w)(x + y + z))'$	12	2.4

Multiple-Operator Standard Logic Gates

Full-adder Design Using XOR Gates

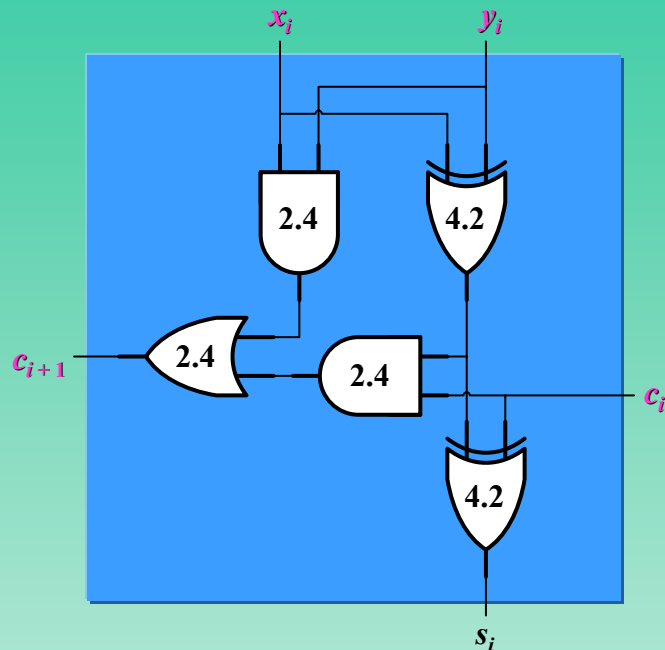

Logic Schematic (46 Transistors)

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth table

Input/Output Path	Delay (ns)
c_i to c_{i+1}	4.8 ns
c_i to s_i	4.2 ns
x_i, y_i to c_{i+1}	9.0 ns
x_i, y_i to s_i	8.4 ns


Full-adder delays

$$\begin{aligned}
 s_i &= x_i'y_i'c_i + x_i'y_ic_i' + x_iy_i'c_i' + x_iy_ic_i \\
 &= (x_i'y_i + x_iy_i')c_i' + (x_i'y_i' + x_iy_i)c_i \\
 &= (x_i \oplus y_i)c_i' + (x_i \odot y_i)c_i \\
 &= (x_i \oplus y_i)c_i' + (x_i \oplus y_i)'c_i \\
 &= (x_i \oplus y_i) \oplus c_i
 \end{aligned}$$

$$\begin{aligned}
 c_{i+1} &= x_iy_ic_i' + x_iy_ic_i + x_i'y_ic_i + x_iy_i'c_i \\
 &= x_iy_i(c_i' + c_i) + c_i(x_i'y_i + x_iy_i') \\
 &= x_iy_i + c_i(x_i \oplus y_i)
 \end{aligned}$$

Full-adder equation

Full-adder Design Using Fast Gates

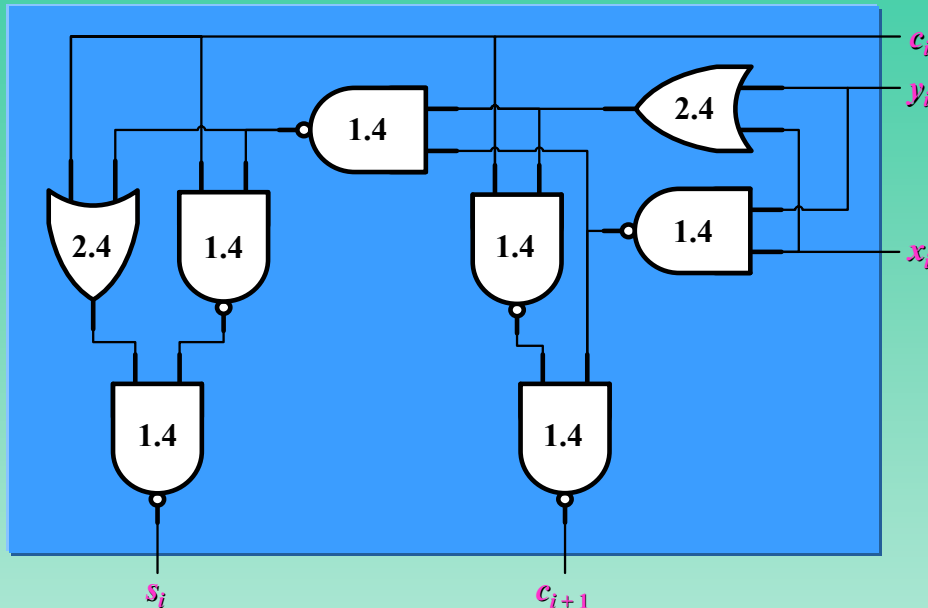

Logic Schematic (36 Transistors)

x_i	y_i	c_i	c_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth table

Input/Output Path	Delay (ns)
c_i to c_{i+1}	2.8 ns
c_i to S_i	3.8 ns
x_i, y_i to c_{i+1}	5.2 ns
x_i, y_i to S_i	7.6 ns

Full-adder delays


$$\begin{aligned}
 x_i \odot y_i &= x_i y_i + x_i' y_i' \\
 &= ((x_i y_i)' (x_i' y_i')')' \\
 &= ((x_i y_i)' (x_i + y_i))'
 \end{aligned}$$

$$\begin{aligned}
 S_i &= (x_i \oplus y_i) c_i' + (x_i \odot y_i) c_i \\
 &= (x_i \odot y_i)' c_i' + (x_i \odot y_i) c_i \\
 &= (x_i \odot y_i) \odot c_i
 \end{aligned}$$

$$\begin{aligned}
 c_{i+1} &= x_i y_i + c_i (x_i + y_i) \\
 &= ((x_i y_i)' (c_i (x_i + y_i)))'
 \end{aligned}$$

Full-adder equation

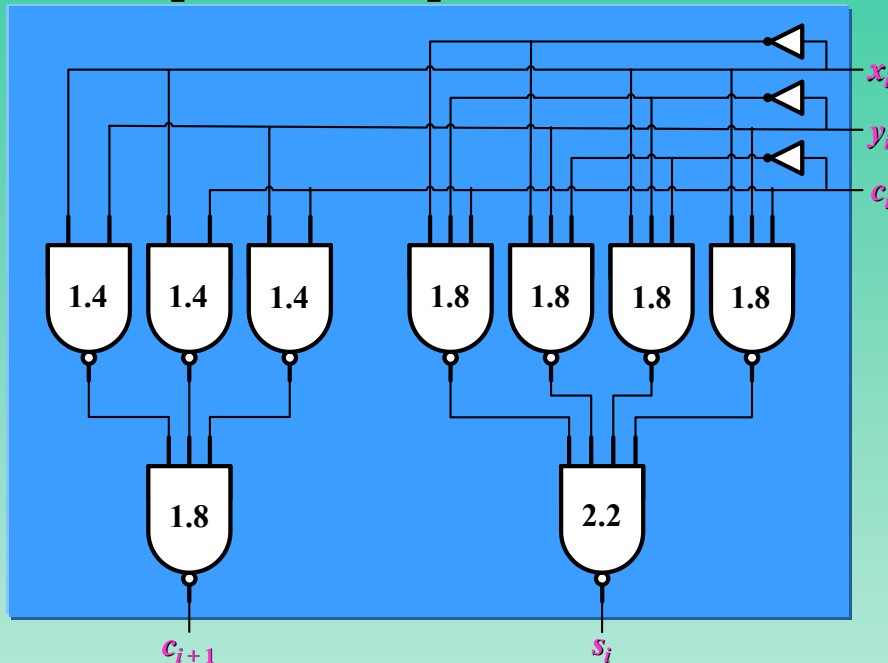Full-adder Design with Multiple-input Gates



Logic Schematic (56 Transistors)

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth table

Input/Output Path	Delay (ns)
c_i to c_{i+1}	3.2 ns
c_i to s_i	5.0 ns
x_i, y_i to c_{i+1}	4.2 ns
x_i, y_i to s_i	5.0 ns

Full-adder delays

$$s_i = x_i'y_i'c_i + x_i'y_i c_i' + x_i y_i' c_i' + x_i y_i c_i$$


$$= ((x_i'y_i'c_i)'(x_i'y_i c_i')'(x_i y_i' c_i')'(x_i y_i c_i))'$$

$$c_{i+1} = x_i y_i + c_i x_i + c_i y_i$$

$$= ((x_i y_i)'(c_i x_i)'(c_i y_i))'$$

Full-adder equation

Full-adder Design with Complex Gates

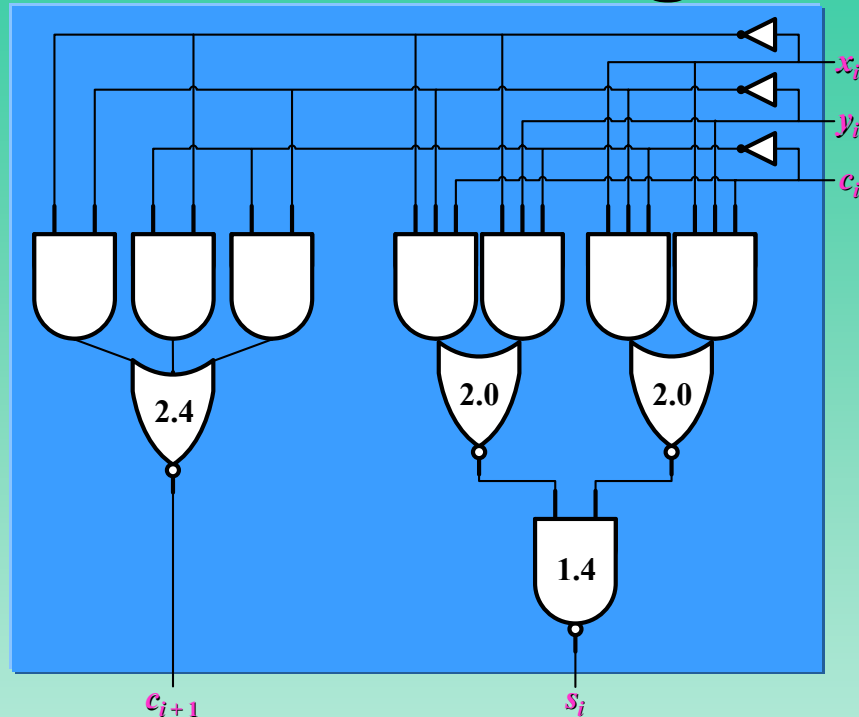

Logic Schematic (46 Transistors)

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth table

Input/Output Path	Delay (ns)
c_i to c_{i+1}	3.4 ns
c_i to s_i	4.4 ns
x_i, y_i to c_{i+1}	3.4 ns
x_i, y_i to s_i	4.4 ns

Full-adder delays

$$s_i = x_i'y_i'c_i + x_i'y_i c_i' + x_i y_i' c_i' + x_i y_i c_i$$

$$= ((x_i'y_i'c_i + x_i'y_i c_i')' (x_i y_i' c_i' + x_i y_i c_i))'$$

$$c_{i+1} = x_i y_i + c_i x_i + c_i y_i$$

$$= ((x_i y_i)' (c_i x_i)' (c_i y_i))'$$

$$= ((x_i' + y_i')(c_i' + x_i')(c_i' + y_i'))'$$

$$= (x_i' y_i' + c_i' x_i' + c_i' y_i)'$$


Full-adder equation

VLSI Technology

- **Small-scale integration (SSI)**
 - ◆ 10 gates/package
- **Medium-scale integration (MSI)**
 - ◆ 10 – 100 gates/package (2 – 4 bit slices)
- **Large-scale integration (LSI)**
 - ◆ 100 – 1000 gates/package (controllers, datapaths, bit slices)
- **Very-large-scale integration (VLSI)**
 - ◆ 1000+ gates/package (systems on a chip)
 - Custom designs (Standard cells)
 - Gate arrays (GAs)
 - Field-programmable (FPGAs)


Custom Design

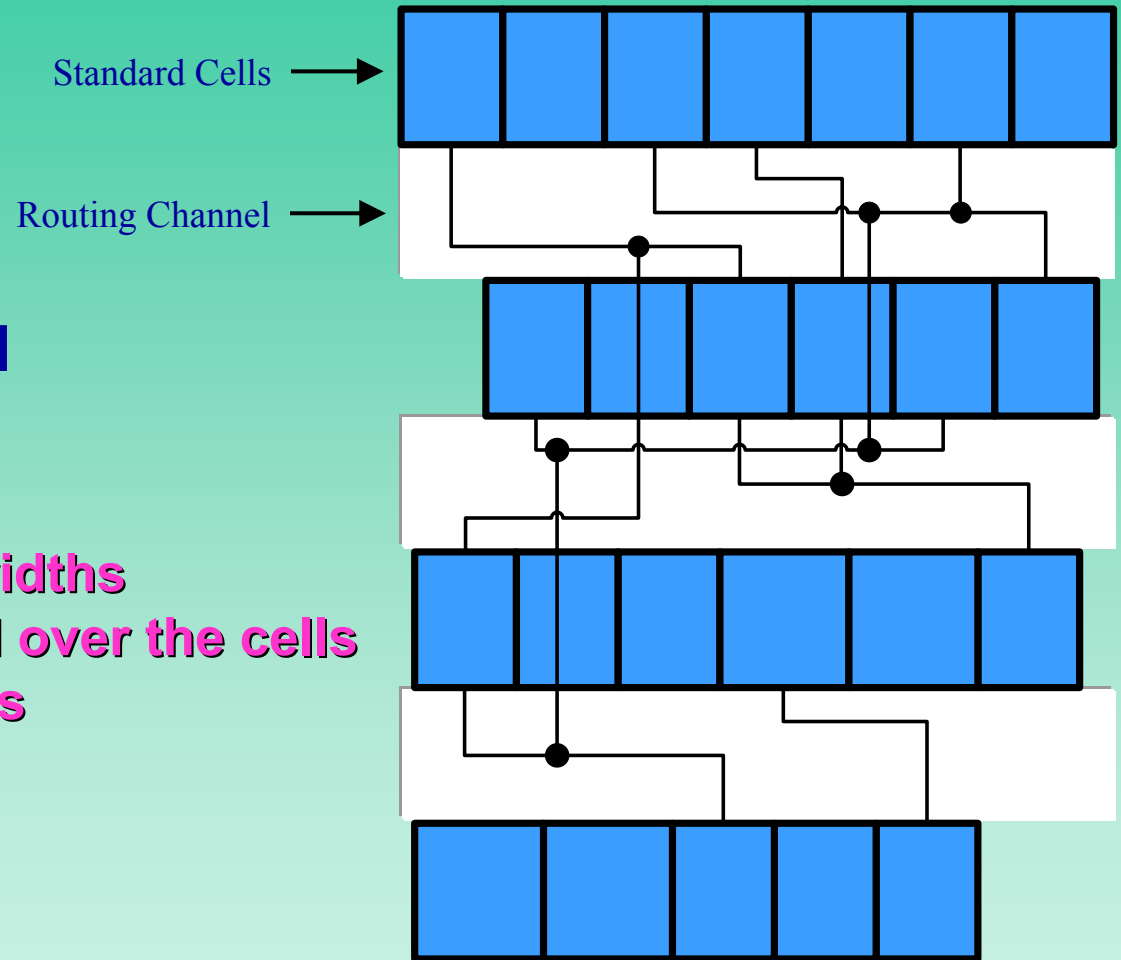- Each designed by hand
- Standard cells
 - ◆ Same height, different widths
 - ◆ Routing in channels and over the cells
 - ◆ Two or more metal layers



Standard Cell Approach


Example of Custom Design

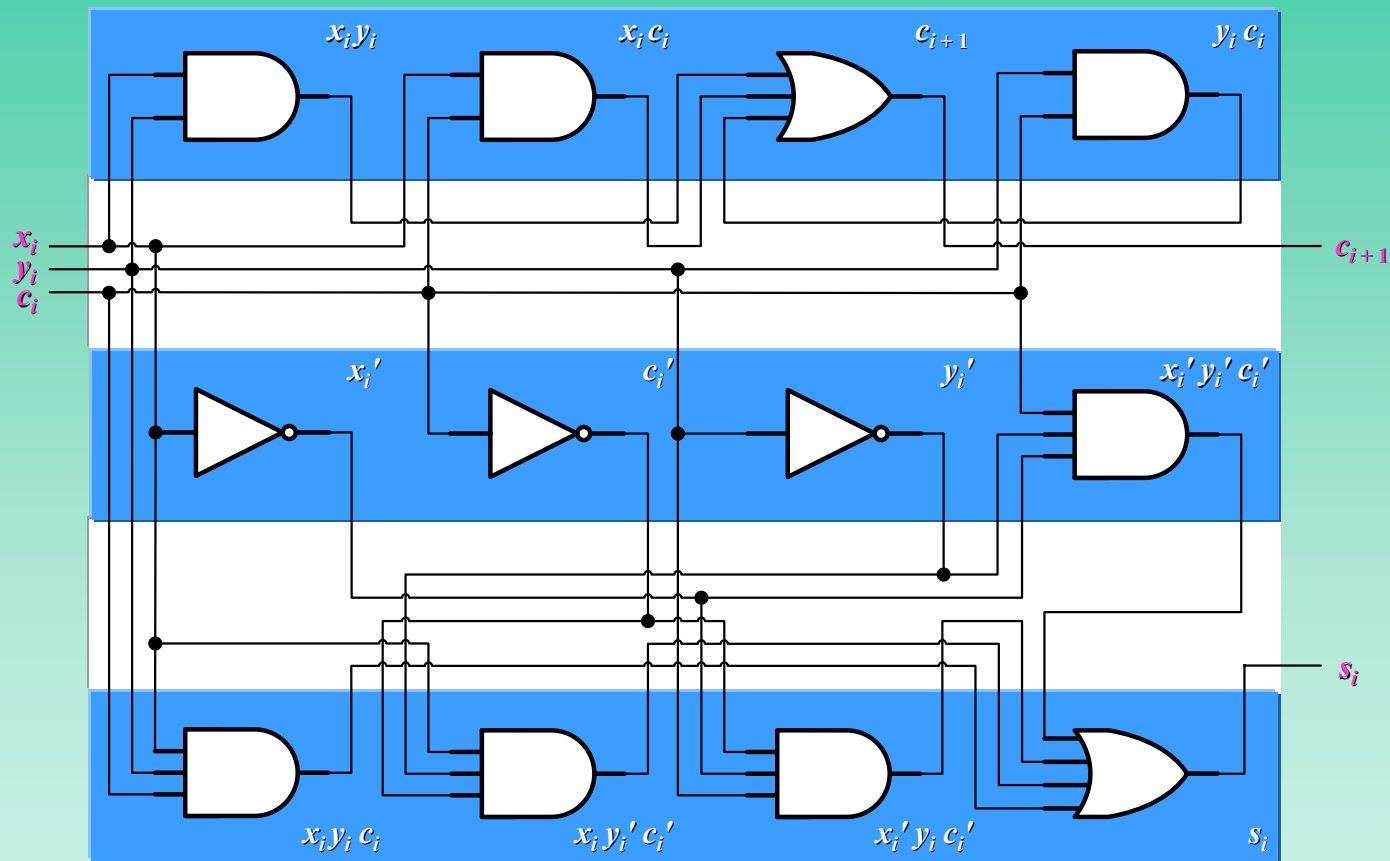

Full-Adder Implementation with Standard Cells

Semi-Custom Approach with Gate Arrays

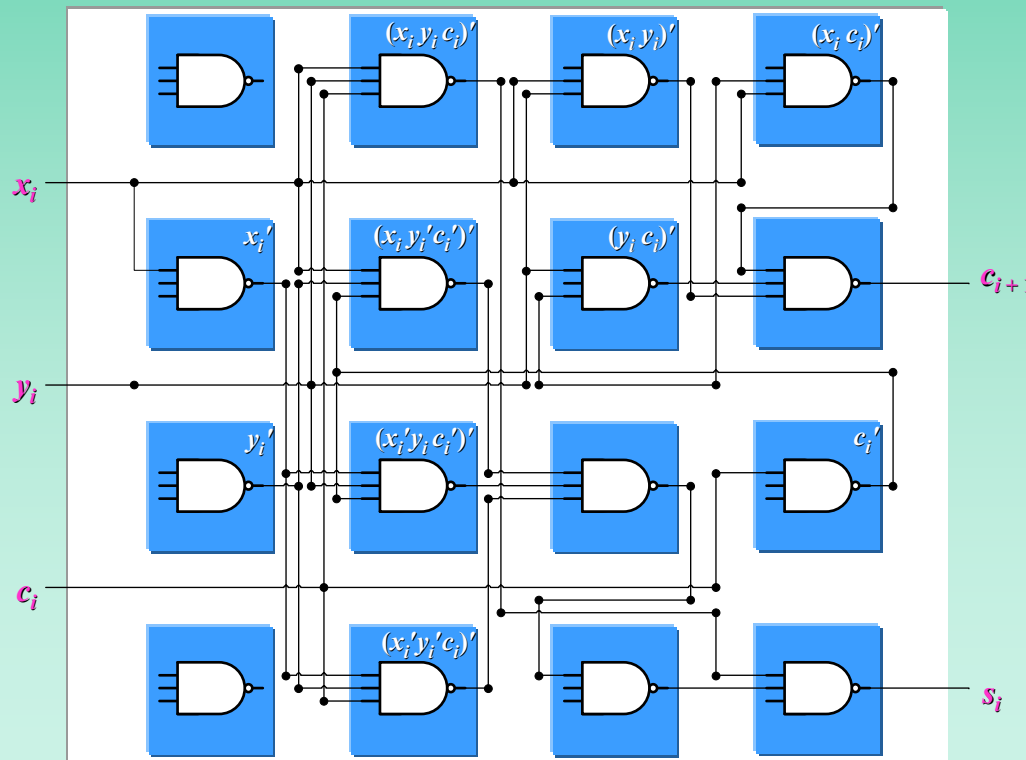
- Gate arrays are prefabricated arrays of interconnected gates
- All gates are the same type (3-input NAND, for example)
- Two or more metal layers used to connect gates




Full-Adder Implementation in a Gate Array

Field-Programmable Approach with FPGA

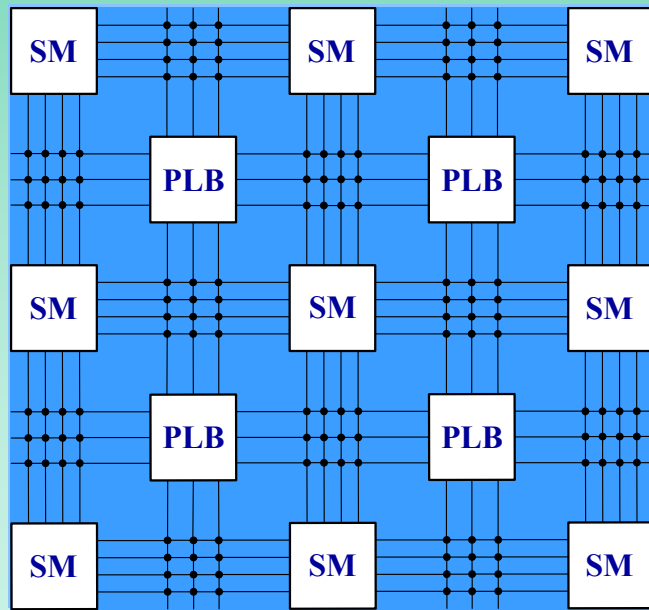
- FPGAs are programmed by loading data into internal memory
- Excellent for rapid prototyping
- Low density and low speed



Array Structure

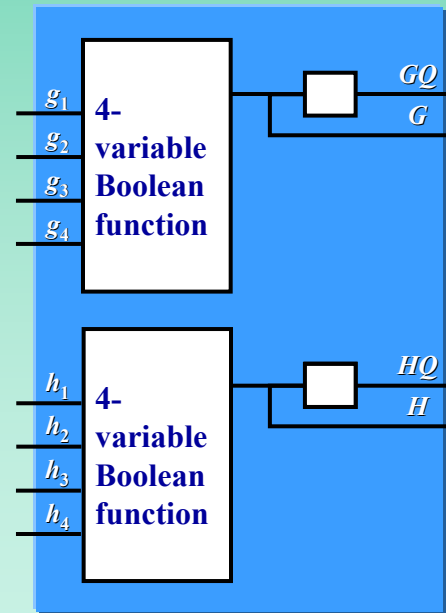


Programmable Logic Blocks (PLB)

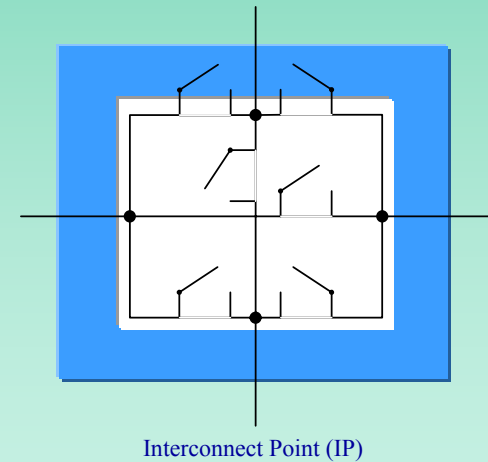

Full-adder Implemented with FPGA

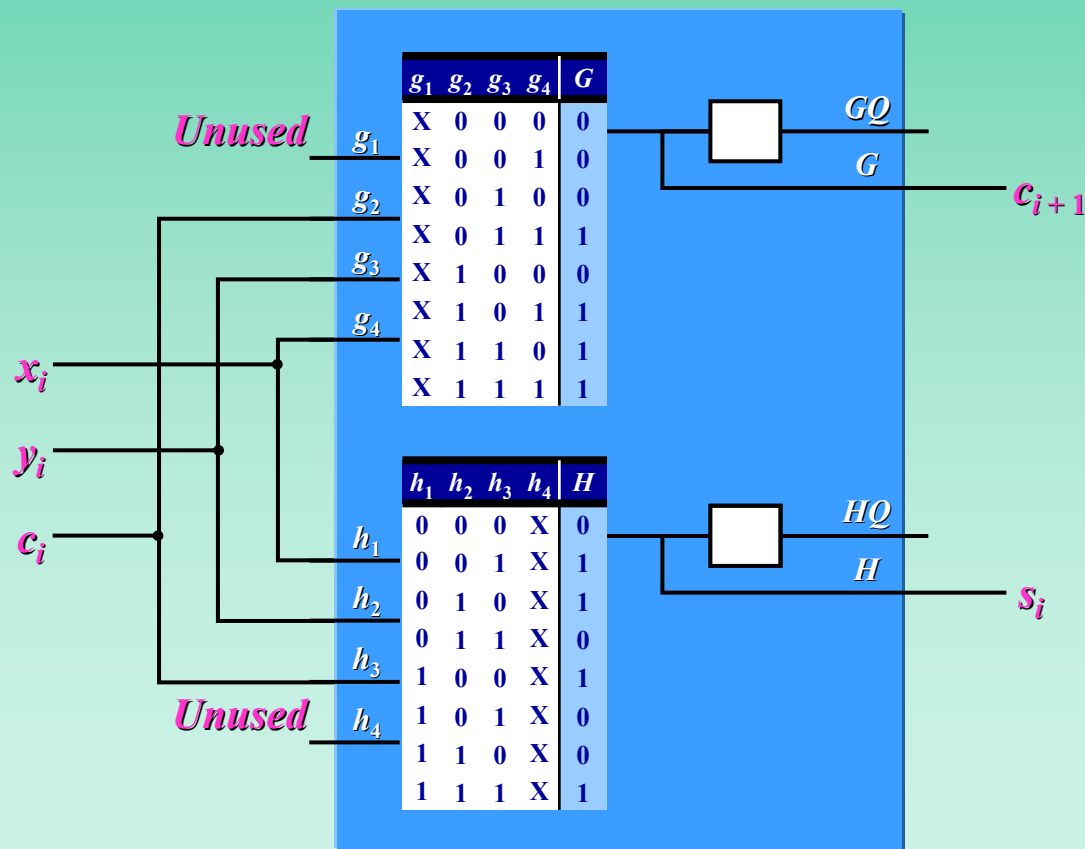- 1 programmable logic block for each full-adder
- 3 out of 4 inputs are used for each Boolean function



Chapter Summary

- **Boolean Algebra**
 - ♦ **Axioms**
 - ♦ **Basic theorems**
- **Boolean Functions**
- **Specification of Boolean Functions**
 - ♦ **Truth tables**
 - ♦ **Algebraic expressions**
 - *Canonical forms*
 - *Standard forms*
 - *Non-standard forms*
- **Algebraic Manipulation of Boolean Expressions**
- **Logic Gates**
 - ♦ **Simple gates**
 - ♦ **Multiple-input gates**
 - ♦ **Complex gates**
- **Implementation Technology**
 - ♦ **SSI (Small-scale integration)**
 - ♦ **MSI (Medium-scale integration)**
 - ♦ **LSI (Large-scale integration)**
 - ♦ **VLSI (Very-large-scale integration)**
 - *Custom designs*
 - *Semi-custom designs*
 - *Field-programmable*