
 


Top-Down Design

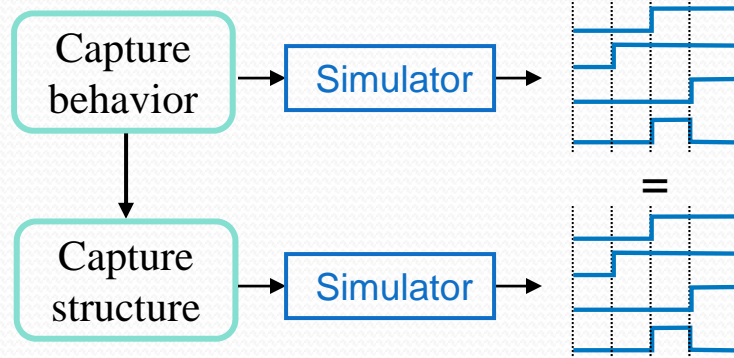

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;


ENTITY Sel2 IS
    PORT (d0, d1: IN std_logic;
          s: IN std_logic;
          Y: OUT std_logic);
END Sel2;

ARCHITECTURE Sel2_beh OF Sel2 IS
BEGIN

    PROCESS(d1, d0, s)
    BEGIN
        IF (s='0') THEN
            Y <= d0;
        ELSE
            Y <= d1;
        END IF;
    END PROCESS;


END Sel2_beh;
```

Behavior to Structure

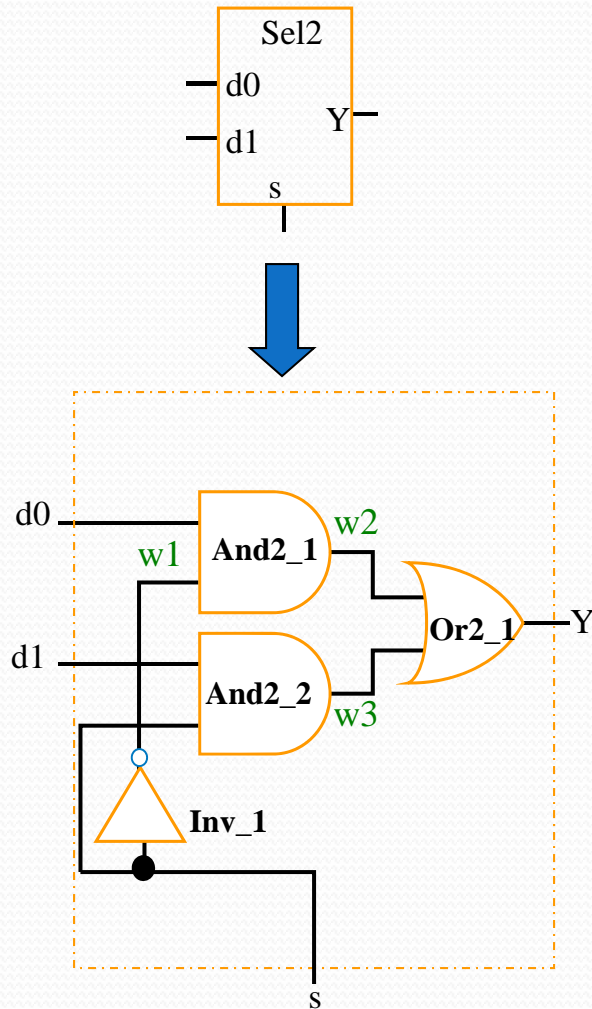

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY Sel2 IS  
    PORT (d1, d0: IN std_logic;  
          s: IN std_logic;  
          Y: OUT std_logic);  
END Sel2;  
-----  
ARCHITECTURE Sel2_str OF Sel2 IS  
    COMPONENT And2 IS  
        PORT (a, b: IN std_logic;  
              F: OUT std_logic);  
    END COMPONENT;  
    COMPONENT Or2 IS  
        PORT (a, b: IN std_logic;  
              F: OUT std_logic);  
    END COMPONENT;  
    COMPONENT Inv IS  
        PORT (a: IN std_logic;  
              F: OUT std_logic);  
    END COMPONENT;  
-----  
    SIGNAL w1, w2, w3: std_logic;  
-----  
BEGIN  
    Inv_1: Inv PORT MAP (s, w1);  
    And2_1: And2 PORT MAP (d0, w1, w2);  
    And2_2: And2 PORT MAP (d1, w1, w3);  
    Or2_1: Or2 PORT MAP (w2, w3, Y);  
END Sel2_str;
```

Simulating Sel2

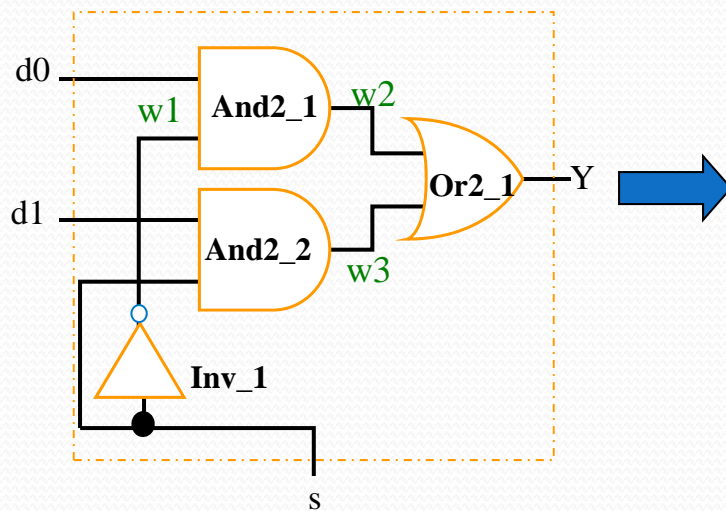

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
ENTITY Testbench IS
END Testbench;
```

```
ARCHITECTURE TBarch OF Testbench IS
  COMPONENT Sel2 IS
    PORT (d1, d0, s: IN std_logic;
          Y: OUT std_logic);
  END COMPONENT;
```

```
  SIGNAL d1_s, d0_s, s_s, Y_s: std_logic;
```

```
BEGIN
```


```
  CompToTest: Sel2
    PORT MAP (d1_s, d0_s, s_s, Y_s);
```

```
PROCESS
BEGIN
```

```
  d1_s <= '0'; d0_s <= '0'; s_s <= '0';
  WAIT FOR 10 ns;
  d1_s <= '0'; d0_s <= '1'; s_s <= '0';
  WAIT FOR 10 ns;
  d1_s <= '0'; d0_s <= '1'; s_s <= '1';
  WAIT FOR 10 ns;
  d1_s <= '1'; d0_s <= '1'; s_s <= '1';
  WAIT FOR 10 ns;
  WAIT;
```

```
END PROCESS;
```

```
END TBarch;
```

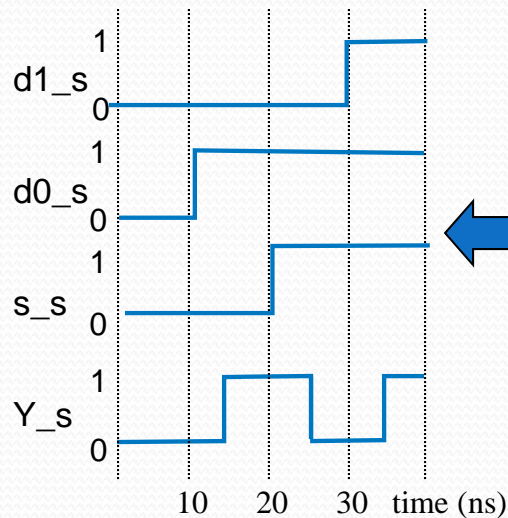

Simulator